

Basic Logic Gates

- Not



where $\bar{x} = \sim x \quad \neg$

- And



where $xy = x \wedge y$

- Or



where $x+y = x \vee y$

- Nand



where $\sim(xy) = \overline{xy}$

- Nor




- Xor



$$\underline{(p \vee q) \wedge (\neg q)}$$

$p, \neg q$


$\neg$	$()$
$\wedge, \vee$	
$\rightarrow$	
$\leftrightarrow$	

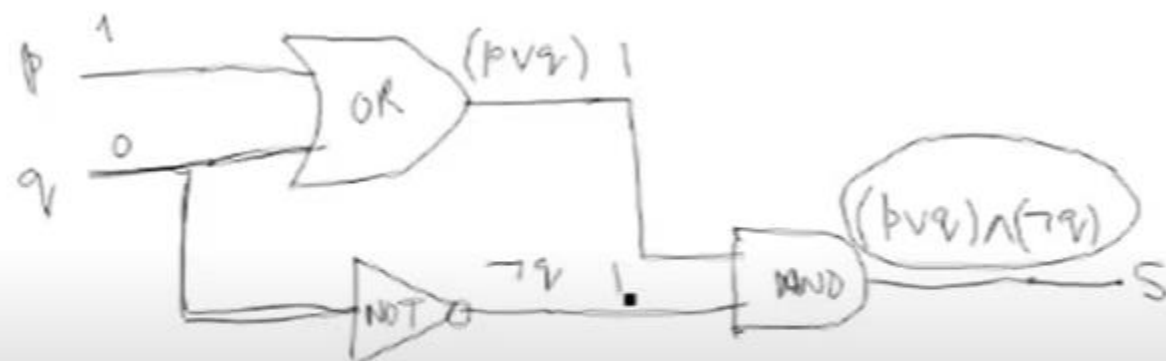

Constructing Circuits

Here is the circuit of the statement

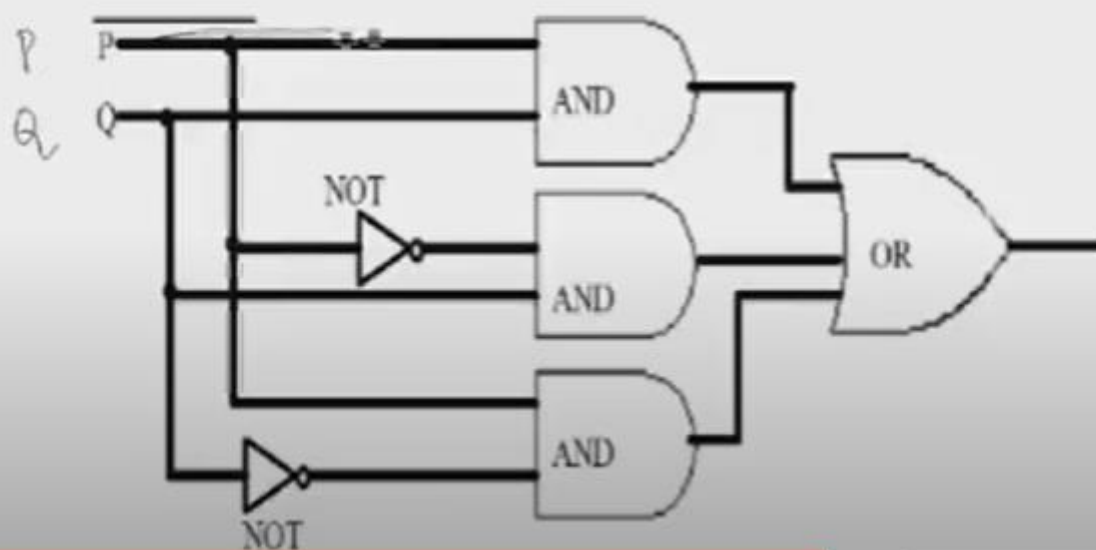
$$(p \wedge q) \vee (\sim p \wedge q) \vee (p \wedge \sim q)$$



Cont...


Following is the circuit output of the following statement
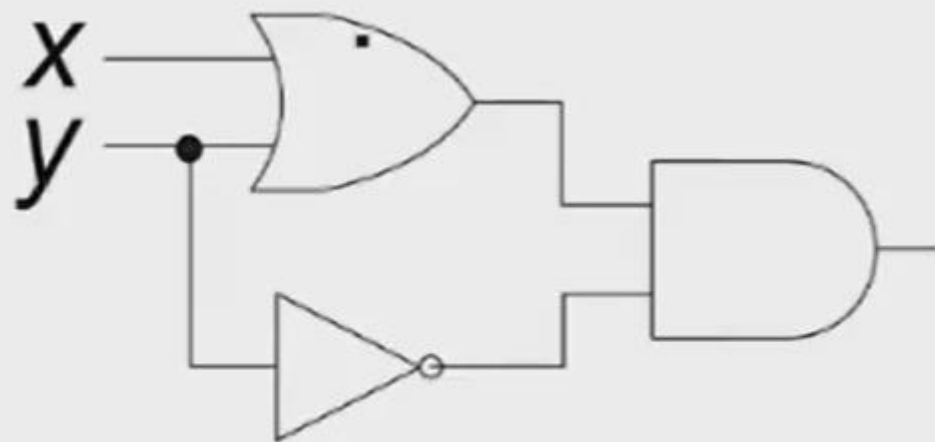
$$(x + y) \wedge \sim y \equiv \underline{(x \vee y)} \wedge \underline{(\neg y)}$$



Switches in series

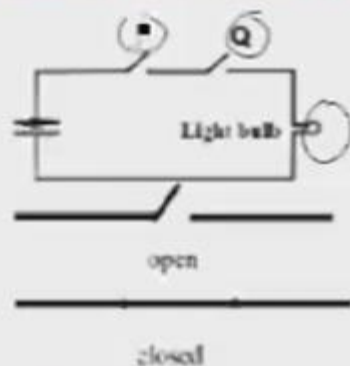- We can see the application of logic in switches:




Switches		Light Bulb
P	Q	State
Closed	Closed	On
Closed	Open	Off
Open	Closed	Off
Open	Open	Off

- Here is the truth table of the switch

P	Q	$P \wedge Q$
T	T	T
T	F	F
F	T	F
F	F	F

Switches in parallel

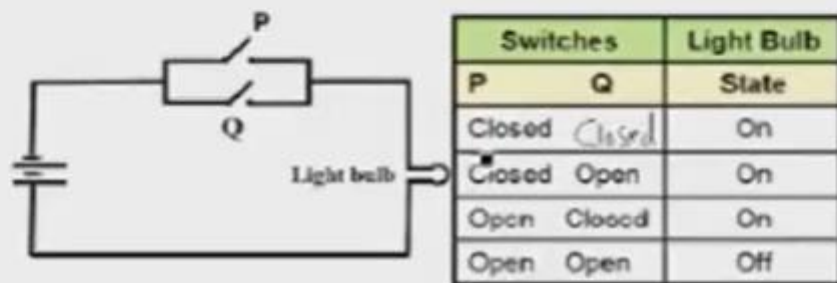- We can see the application of logic in switches:



- Here is the truth table of the switch:

P	Q	$P \vee Q$
T	T	T
T	F	T
F	T	T
F	F	F

Designing a circuit for a given input/output

Here is the out put

P, Q, R

INPUTS			OUTPUT
P	Q	R	S
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0

we can write it as following

INPUTS			OUTPUT
P	Q	R	S
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0

→ $P \wedge Q \wedge \neg R$

→ $\neg P \wedge Q \wedge R$


Designing a circuit for a given input/output

$$(P \wedge Q \wedge \neg R) \vee (\neg P \wedge Q \wedge R)$$

P, Q, R .

- Here is the circuit of the previous input/output

CIRCUIT DIAGRAM:

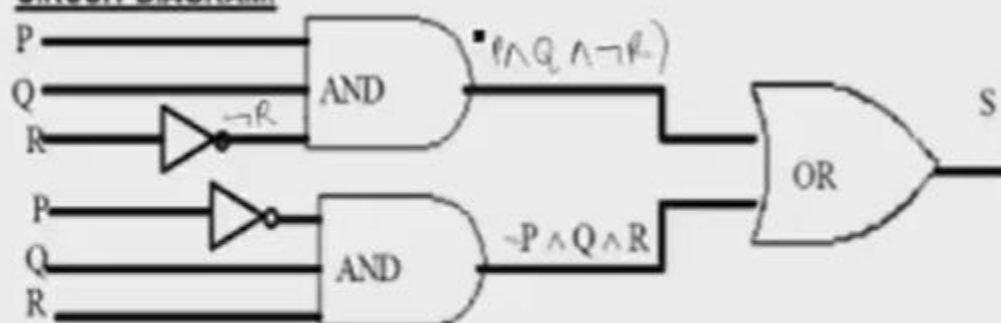

Circuit reductions

Following is the circuit representations of the statement

$$(P \wedge Q) \vee (\neg P \wedge Q) \vee (P \wedge \neg Q)$$

